


Arbeitsblatt:

Kennziffer des Prüfungsteilnehmers: _____

zu 6.1

Eingänge			Ausgänge	
C	B	A	S	Ü

zu 6.4

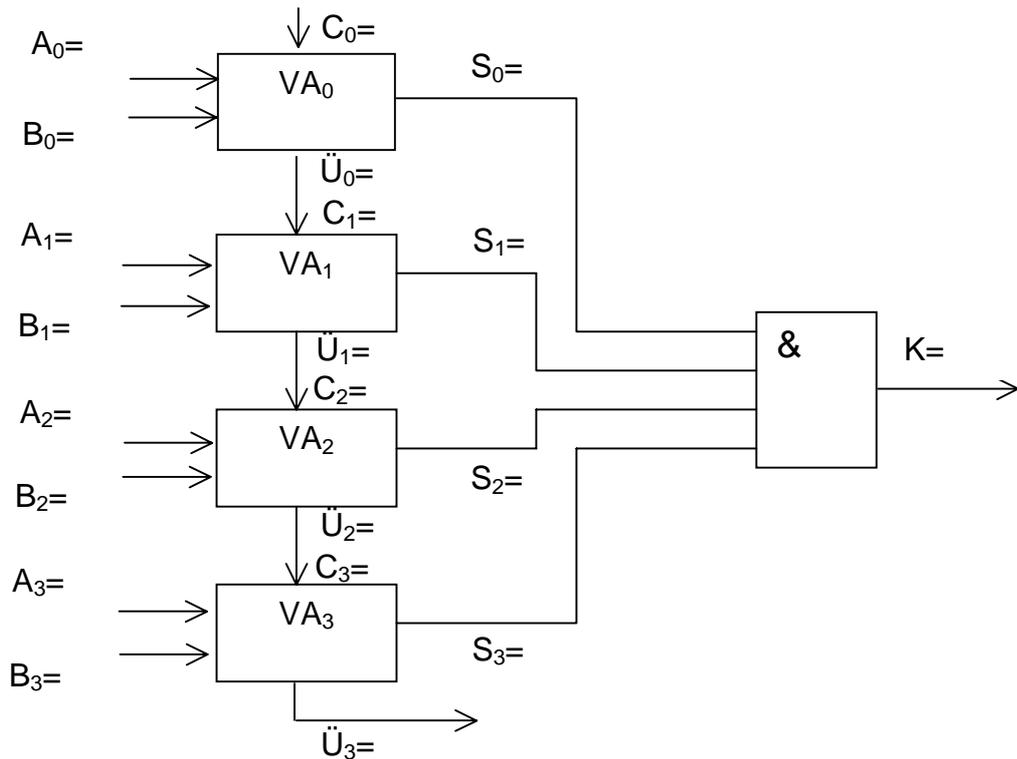

zu 6.5

VA ₀					VA ₁					VA ₂					VA ₃				
A ₀	B ₀	C ₀	S ₀	Ü ₀	A ₁	B ₁	C ₁	S ₁	Ü ₁	A ₂	B ₂	C ₂	S ₂	Ü ₂	A ₃	B ₃	C ₃	S ₃	Ü ₃